

ECE 110 Cramming Carnival Review

Author: Members of HKN


Fall 2024

Introduction

This worksheet does not cover content in lectures after November 25th and is not meant to be a replacement for any practice exams or section reviews. Use this worksheet as a quick refresher for various topics throughout the semester and for slightly different questions than the homeworks.

Formulas not on the help sheet

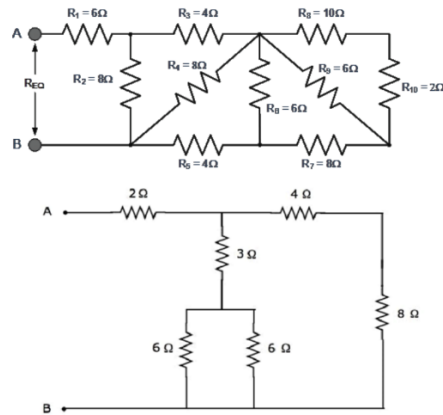Note: All formulas required for the questions are assumed to be known, as they are not provided in this sheet.



Power Efficiency & Capacitors


Question 1: Consider a car that has 400 kJ of energy at a specific speed. The car's regenerative brakes are 40% efficient at converting kinetic energy to energy stored in a battery. What is the energy added when the car brakes to half speed?

Question 2: If a 15 kWh battery has to be recharged using a 60% efficient generator with peak power of 500 W, how long does the generator need to run to fully charge the battery?


Question 3: What is the energy stored in a 4 nF capacitor charged to 9V?

Question 4: What voltage is needed to charge the capacitor from the above question enough to lift a 2-gram mass 15 cm?


Kirchoff's Laws/Dividers

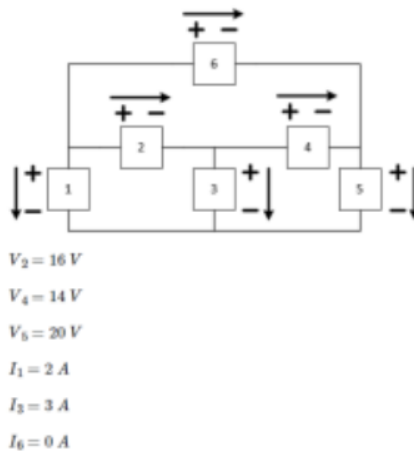

Question 5: Given the above circuit and information, find V_1 , V_3 , V_6 , I_2 , I_4 , and I_5 .

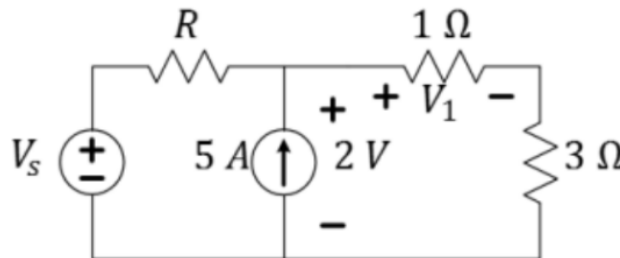

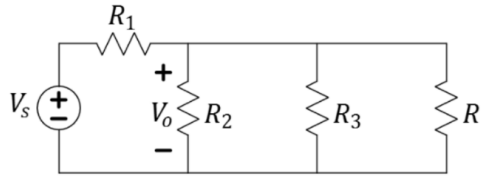Question 6: Find V_1 in the above circuit.




$$R_1 = 9 \, \Omega$$

$$R_2 = 10 \, \Omega$$

$$R_3 = 15 \, \Omega$$

$$V_s = 4 \, V$$


Question 7: What value of R will result in $V_o = 1 \, V$?

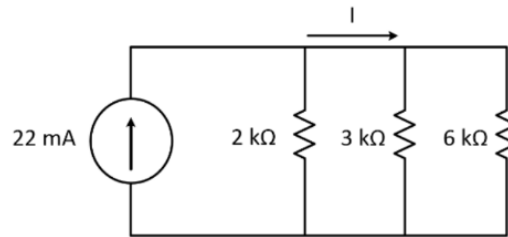

Question 8: Find I in the above circuit.

Equivalent Resistance / Power

Question 9: Find equivalent resistance for the circuits below.

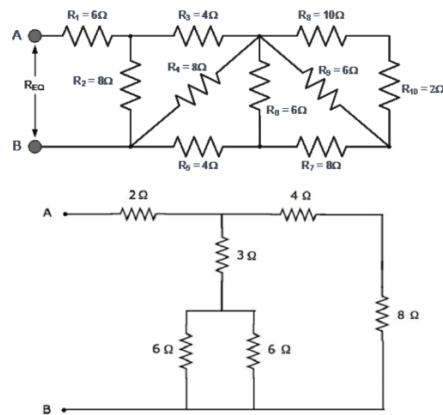

Question 10: If the voltage between nodes A and B in the second circuit is $9 \, V$...


1. What is the current through the 3 ohm resistor?
2. What is the power through the 3 ohm resistor?
3. What is the power through the 8 ohm resistor?
4. What resistor has the highest power output?

PWM

Question 11: Imagine a square wave that outputs 15W from 0 to 12 seconds and 5W from 12 to 20 seconds. This square wave corresponds to a 10 ohm resistor.


1. What is the Average Power of this waveform?
2. What is the RMS Voltage of this waveform?

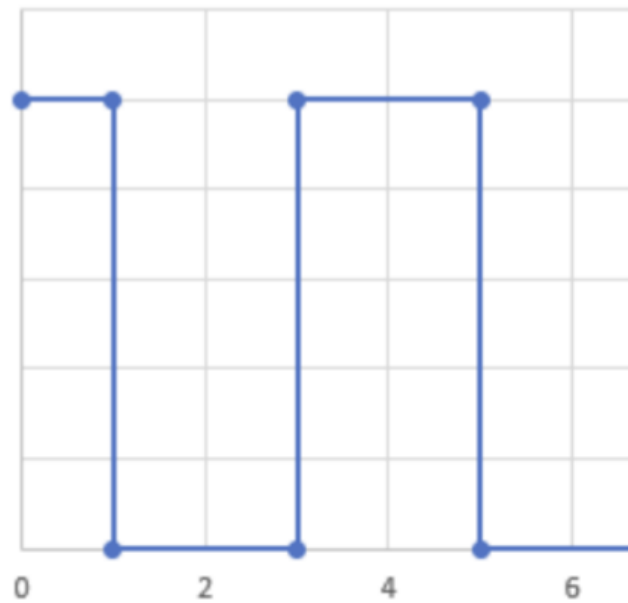Question 12: Given a limited portion of this graphed waveform, what is its duty cycle?




I-V Equations

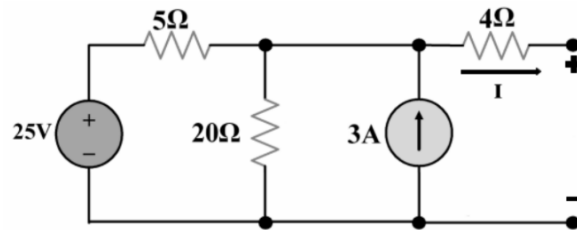Question 13: What is the short circuit current and the open circuit voltage for the circuit below?



Question 14: If this circuit were to be placed in series with another circuit with an IV equation of $I = 0.005V - 0.025$, assuming the same polarities given above, what would be the operating current and voltage?

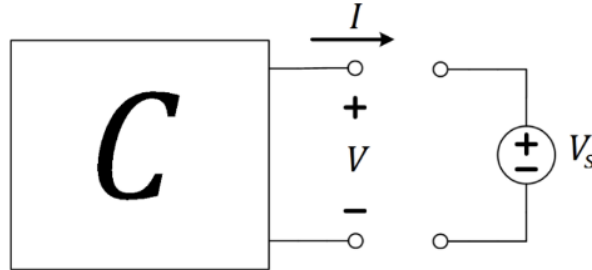Question 15: If the open circuit voltage of a circuit containing ideal sources and resistors is measured at $V_{oc} = 8\text{ V}$, while the current through the short circuit across the circuit is $I_{sc} = 200\text{ mA}$, what would be the power in watts absorbed by an ideal voltage source, $V_s = 4$, placed across the terminals?




Norton and Thevenin

Question 16: Give Norton and Thevenin Forms for the subcircuit shown on the previous page.

Question 17: What is the Norton resistance of the circuit below? What is the Thevenin Resistance?

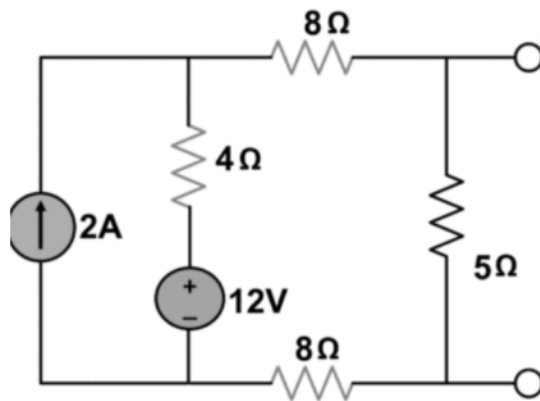
Question 18: Draw the Thevenin and Norton Equivalents.



Nodal Analysis


Question 19: Find the voltage at node A for this circuit.

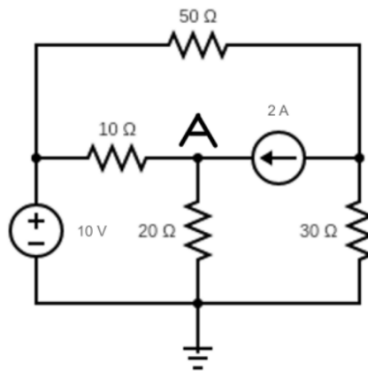Question 20: Find the voltage drop across the 10, 30, and 50 ohm resistors.



Diodes

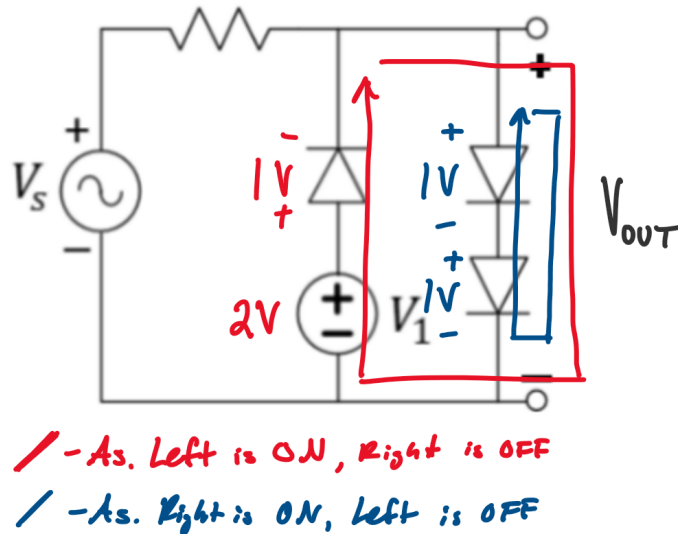Question 21: Assume an ideal-offset model and $V_{on} = 1$ volt. If $V_s = 5 \cos(\omega t)$ volts and $V_1 = 2$ volts, what are the maximum and minimum voltages across the open nodes?



Solution: Both branches of the diode cannot be ON at the same time, as if positive current flows through one, negative current would flow through the other (which is impossible). We start by solving for V_{out} assuming one diode configuration is ON (below, we start with the left branch) while the other is OFF.

KVL Loops are shown above with assumptions the Voltage source has extremes high or low enough that they will conduct current.

$$V_{out} = 2V - 1V = 1V.$$

For current to flow in the correct direction, the voltage on the right of the resistor must have a larger value than the voltage on the left. We have determined $V_{out} = 1V$, we now check whether V_s can be smaller than that number.

$$V_{S \min} = -5V < 1V \Rightarrow \boxed{V_{out \min} = 1V}$$


Restart this process with the KVL loop with the right branch of diodes.

$$V_{out} = 1V + 1V = 2V$$

Current must flow in the resistor from left to right to satisfy the diode assumption. Find a value of V_s that is greater than our calculated V_{out}

$$V_{S \max} = 5 > 2V \Rightarrow \boxed{V_{out \max} = 2V}$$

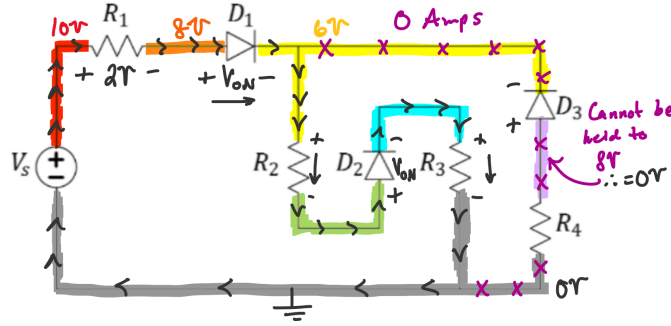Question 22: In the circuit below, which diodes are on? Furthermore, if $V_S = 10\text{ V}$, all the diodes have $V_{ON} = 2\text{ V}$ under the offset ideal model, and the voltage drop over R_1 is also 2 V , what is the voltage drop across the other resistors, assuming they have an equal resistance?



Solution:

When looking at D_3 , we notice two things:

- The **positive** terminal of D_3 is connected to the **negative** terminal of V_S through a resistor.
- There is only one source of power in the circuit (V_S). (Because of this, the smallest nodal voltage that any node could be held at is 0 V (the negative terminal of the V_S))


Thus, it is impossible for the voltage difference across the diode, V_{D_3} , to be greater than 0 V . In fact, if we assume D_1 to be on, we can calculate that $V_{yellow} = V_S - V_{R_1} - V_{ON} = 6\text{ V}$. V_{pink} would need to be 2 V greater than V_{yellow} in order for D_3 to turn on. Since a resistor is a passive component (adds no power to the circuit), it is impossible to raise the pink node to above $6\text{ V} + 2\text{ V} = 8\text{ V}$, which would allow D_3 to turn on.

Since D_3 is not conducting any current, $I_{R_1} = I_{R_2} = I_{R_3} = I_{D_1} = I_{D_2} > 0\text{ A}$. We know the currents will be positive since R_1 's voltage drop is positive and moving away from the voltage source (no other supply of power in the circuit). Because the currents are all positive, we can conclude that D_1 and D_2 are ON. For any two resistors of equal resistance and equal current, we know that their voltage drops must also be equal. Algebraically, we can show this as follows:

$$\begin{aligned}
 I_{R_1} &= I_{R_2} = I_{R_3} \\
 \text{Using Ohm's Law: } \frac{2\text{ V}}{R} &= \frac{V_{R_2}}{R} = \frac{V_{R_3}}{R} \\
 2\text{ V} &= V_{R_2} = V_{R_3} \\
 V_{R_2} &= \boxed{2\text{ V}} \\
 V_{R_3} &= \boxed{2\text{ V}}
 \end{aligned}$$

BJTs



Question 23: The properties of the transistor are that V_{BE} on is 1V, β is 120, and $V_{CE\text{ sat}}$ is 0.2 V. In this circuit, V_{CC} is 9V, R_C is 150Ω , and R_B is 30000Ω . What are the maximum and minimum values for V_{CE} if V_i 's output is variable between 0V and 9V?

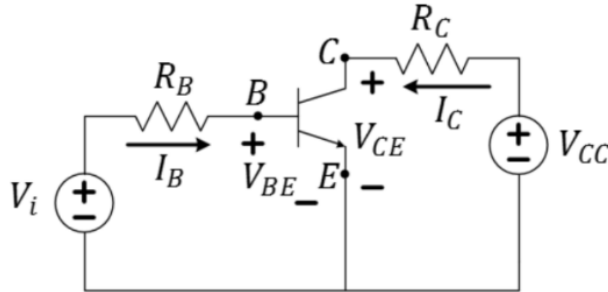

Question 24: If V_i was set to 5V, what would V_{CE} be?

MOSFETs/cMOS logic

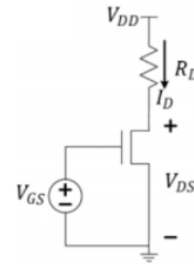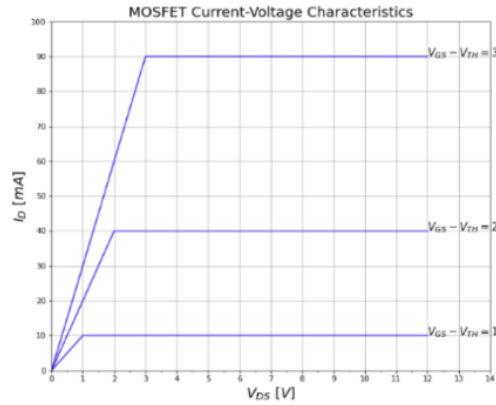Question 25: An IC dissipates 110W. If the IC has a 5% activity factor α , frequency of 10GHz, and 1nF gate capacitance, what is the maximum number of transistors that can be in the IC if it can operate at up to 9V?



Question 26: The given circuit with a MOSFET in series with a voltage source of 6V and a resistor with a resistance of 120Ω . Find the transistor parameter k and a value for V_{DS} that results in $I = 30$ mA, given that $V_{GS} - V_{TH} = 2$.

Bonus Questions

Question 27: Give the IV equation, Norton equivalent, and Thevenin Equivalent for the circuit below.

