

# ECE 110 Cramming Carnival Review

Author: Members of HKN


Fall 2024

## Introduction

This worksheet does not cover content in lectures after November 25th and is not meant to be a replacement for any practice exams or section reviews. Use this worksheet as a quick refresher for various topics throughout the semester and for slightly different questions than the homeworks.
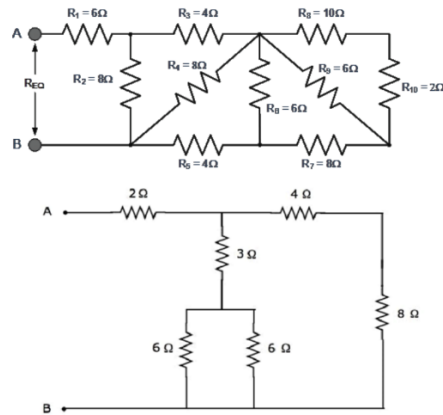
## Formulas not on the help sheet

**Note:** All formulas required for the questions are assumed to be known, as they are not provided in this sheet.



## Power Efficiency & Capacitors


**Question 1:** Consider a car that has 400 kJ of energy at a specific speed. The car's regenerative brakes are 40% efficient at converting kinetic energy to energy stored in a battery. What is the energy added when the car brakes to half speed?

**Question 2:** If a 15 kWh battery has to be recharged using a 60% efficient generator with peak power of 500 W, how long does the generator need to run to fully charge the battery?


**Question 3:** What is the energy stored in a 4 nF capacitor charged to 9V?

**Question 4:** What voltage is needed to charge the capacitor from the above question enough to lift a 2-gram mass 15 cm?


## Kirchoff's Laws/Dividers

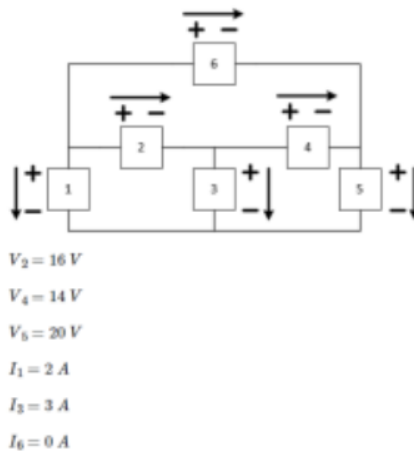

**Question 5:** Given the above circuit and information, find  $V_1$ ,  $V_3$ ,  $V_6$ ,  $I_2$ ,  $I_4$ , and  $I_5$ .

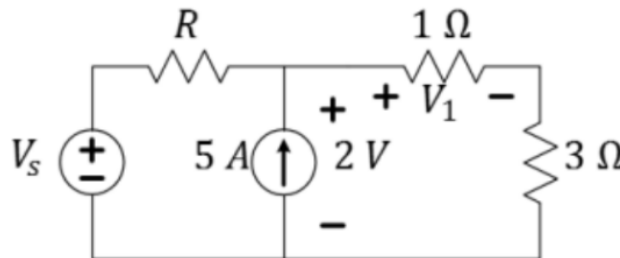

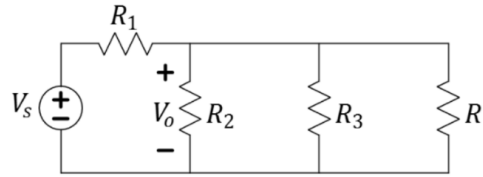**Question 6:** Find  $V_1$  in the above circuit.




$$R_1 = 9 \, \Omega$$

$$R_2 = 10 \, \Omega$$

$$R_3 = 15 \, \Omega$$

$$V_s = 4 \, V$$


**Question 7:** What value of  $R$  will result in  $V_o = 1 \, V$ ?

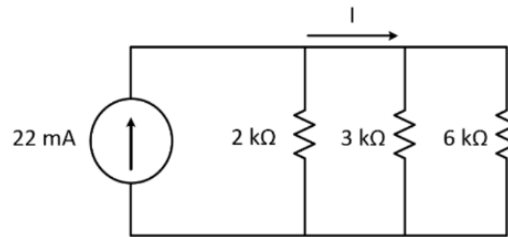

**Question 8:** Find  $I$  in the above circuit.

## Equivalent Resistance / Power

**Question 9:** Find equivalent resistance for the circuits below.

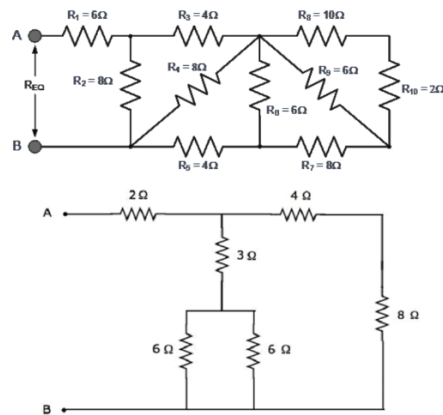

**Question 10:** If the voltage between nodes  $A$  and  $B$  in the second circuit is  $9 \, V$ ...


1. What is the current through the 3 ohm resistor?
2. What is the power through the 3 ohm resistor?
3. What is the power through the 8 ohm resistor?
4. What resistor has the highest power output?

## PWM

**Question 11:** Imagine a square wave that outputs 15W from 0 to 12 seconds and 5W from 12 to 20 seconds. This square wave corresponds to a 10 ohm resistor.


1. What is the Average Power of this waveform?
2. What is the RMS Voltage of this waveform?

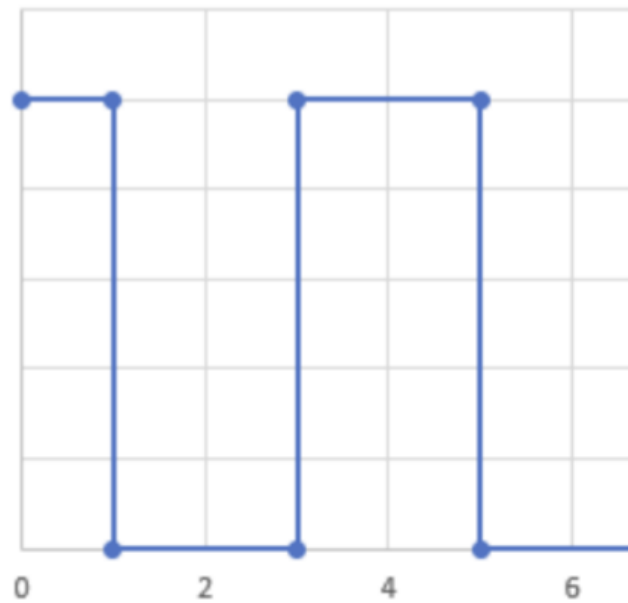**Question 12:** Given a limited portion of this graphed waveform, what is its duty cycle?




## I-V Equations

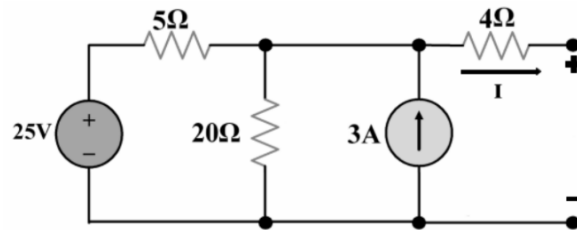**Question 13:** What is the short circuit current and the open circuit voltage for the circuit below?



**Question 14:** If this circuit were to be placed in series with another circuit with an IV equation of  $I = 0.005V - 0.025$ , assuming the same polarities given above, what would be the operating current and voltage?

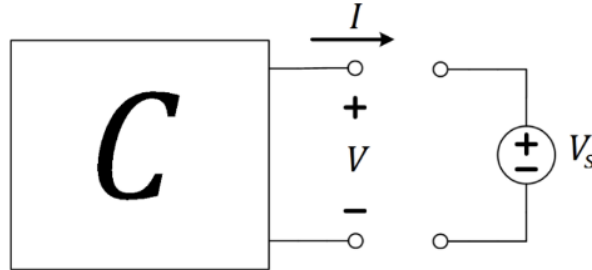**Question 15:** If the open circuit voltage of a circuit containing ideal sources and resistors is measured at  $V_{oc} = 8\text{ V}$ , while the current through the short circuit across the circuit is  $I_{sc} = 200\text{ mA}$ , what would be the power in watts absorbed by an ideal voltage source,  $V_s = 4$ , placed across the terminals?




## Norton and Thevenin

**Question 16:** Give Norton and Thevenin Forms for the subcircuit shown on the previous page.

**Question 17:** What is the Norton resistance of the circuit below? What is the Thevenin Resistance?

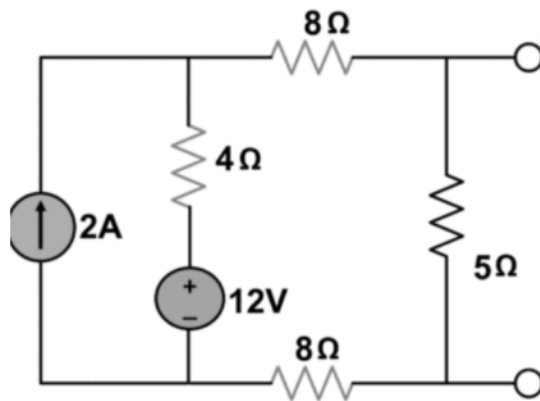
**Question 18:** Draw the Thevenin and Norton Equivalents.



## Nodal Analysis


**Question 19:** Find the voltage at node A for this circuit.

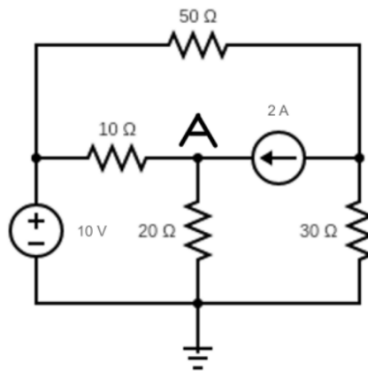**Question 20:** Find the voltage drop across the 10, 30, and 50 ohm resistors.



## Diodes

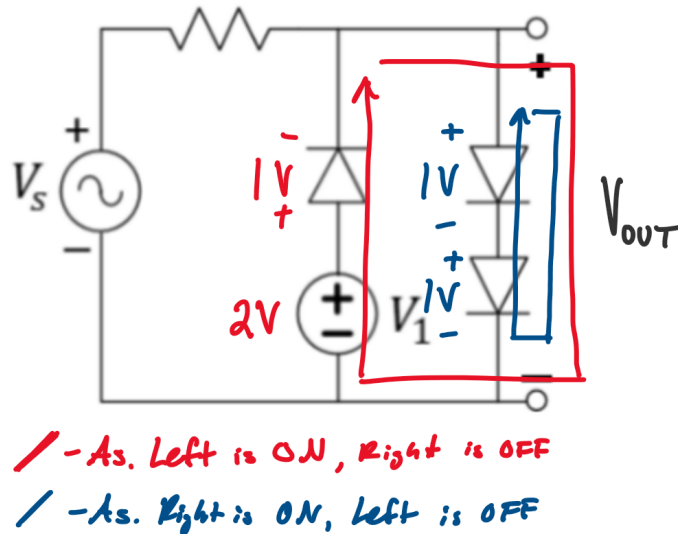**Question 21:** Assume an ideal-offset model and  $V_{on} = 1$  volt. If  $V_s = 5 \cos(\omega t)$  volts and  $V_1 = 2$  volts, what are the maximum and minimum voltages across the open nodes?



**Solution:** Both branches of the diode cannot be ON at the same time, as if positive current flows through one, negative current would flow through the other (which is impossible). We start by solving for  $V_{out}$  assuming one diode configuration is ON (below, we start with the left branch) while the other is OFF.

KVL Loops are shown above with assumptions the Voltage source has extremes high or low enough that they will conduct current.

$$V_{out} = 2V - 1V = 1V.$$

For current to flow in the correct direction, the voltage on the right of the resistor must have a larger value than the voltage on the left. We have determined  $V_{out} = 1V$ , we now check whether  $V_s$  can be smaller than that number.

$$V_{S \min} = -5V < 1V \Rightarrow \boxed{V_{out \min} = 1V}$$


Restart this process with the KVL loop with the right branch of diodes.

$$V_{out} = 1V + 1V = 2V$$

Current must flow in the resistor from left to right to satisfy the diode assumption. Find a value of  $V_s$  that is greater than our calculated  $V_{out}$

$$V_{S \max} = 5 > 2V \Rightarrow \boxed{V_{out \max} = 2V}$$

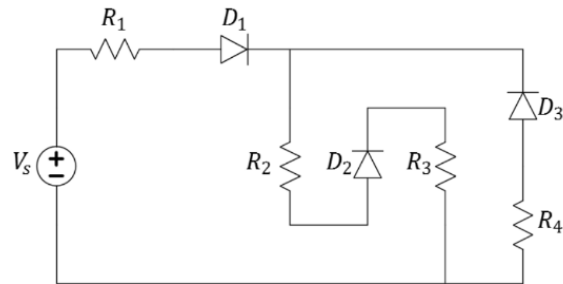
**Question 22:** In the circuit below, which diodes are on? Furthermore, if  $V_s = 10\text{ V}$ , all the diodes have  $V_{on} = 2\text{ V}$  under the offset ideal model, and the voltage drop over  $R_1$  is also  $2\text{ V}$ , what is the voltage drop across the other resistors, assuming they have an equal resistance?





## BJTs



**Question 23:** The properties of the transistor are that  $V_{BE}$  on is 1V,  $\beta$  is 120, and  $V_{CE\text{ sat}}$  is 0.2 V. In this circuit,  $V_{CC}$  is 9V,  $R_C$  is  $150\Omega$ , and  $R_B$  is  $30000\Omega$ . What are the maximum and minimum values for  $V_{CE}$  if  $V_i$ 's output is variable between 0V and 9V?

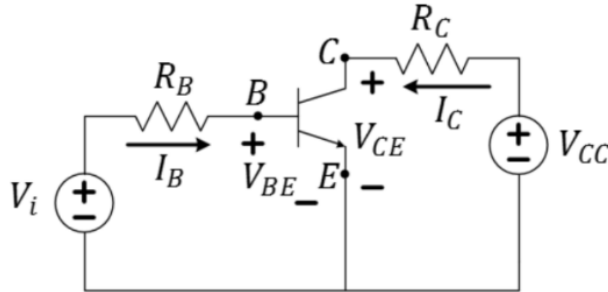

**Question 24:** If  $V_i$  was set to 5V, what would  $V_{CE}$  be?

## MOSFETs/cMOS logic

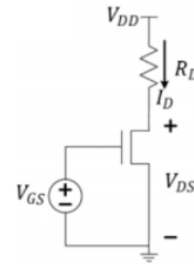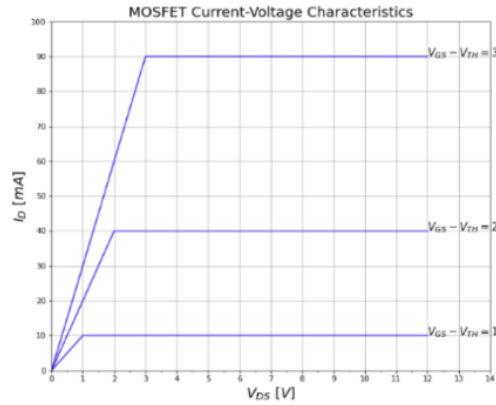**Question 25:** An IC dissipates 110W. If the IC has a 5% activity factor  $\alpha$ , frequency of 10GHz, and 1nF gate capacitance, what is the maximum number of transistors that can be in the IC if it can operate at up to 9V?



**Question 26:** The given circuit with a MOSFET in series with a voltage source of 6V and a resistor with a resistance of  $120\Omega$ . Find the transistor parameter  $k$  and a value for  $V_{DS}$  that results in  $I = 30$  mA, given that  $V_{GS} - V_{TH} = 2$ .

## Bonus Questions

**Question 27:** Give the IV equation, Norton equivalent, and Thevenin Equivalent for the circuit below.

